

BIM / Second Semester / IT 233: Digital Logic

*Candidates are required to answer the questions in **their own words as far as practicable.***

Brief Answer

Questions:

1. What is digital system?

Group "A"

[10 × 1=10]

2

How many different combination can be represented by 5-bit binary data?

3.

What is the use of Karnaugh Map?

4 . How many input lines are required to generate 995 decoded lines?

Differentiate between combinational and sequential circuit.

5.

6.

What is the problem of "T" flip-flop?

7.

What is the number of clock pulses required to input and output "5" bit data in parallel in serial out shift register?

8.

Define don't case condition.

-9.

How many don't case condition are possible in 8 x 3 encoder?

10. Why flip flop is said to be 1 bit memory?
flop is sai

Group "B"

Short Answer *Questions*: (Attempt any **FIVE Questions**)

11. Convert **2A3B.2A16** into binary, octal and decimal.

12. Realize the property of **AND**, **OR** and **NOT** gate using **NAND** gate.

[5×3=15]

13. If a **Boolean function** $F = xy + xy + xyz$, solve the given function using **K-map**.

14. **Design** 4×1 multiplexer.

15. **Explain** triggering of a flip-flop with its types.

If a **Boolean function** $F = AB + BC$, find a equivalent POS.

Group "C"

Long Answer Questions: (Attempt any **THREE Questions**)

1. **What** is **gray code**? **Design** 3-bit synchronous counter.

[3×5=15]

18. You are provided with data bits 1011. The register provided has the capability to store all bits in one clock pulse and can be retrieved those stored bits only one at a time from right most flip flop. Your work is to draw the circuit and show all necessary steps to store and retrieve the provided data in provided register.

19. Design a circuit diagram of a 3-bit parallel

adder.

20 What is the advantage of JK flip flop over clocked SR flip flop? Explain the operational characteristics of JK flip flop with logic diagram.

Group “D”

Comprehensive Answer / Case / Situation Analysis

Questions:

[2×10=20]

21. What is Boolean algebra? List any five Boolean rules and verify any two Boolean rules using truth table method.

22. Differentiate between PLA and ROM. Design MOD-150 asynchronous counter.

2022 AD admitted
Regular Students

FACULTY OF MANAGEMENT

Office of the Dean

October 2023

BIM / Second Semester/IT 233: Digital Logic

Pass Marks: 30

Time: 3 Hrs.

Candidates are *required* to answer the *questions in their own words* as far as practicable.

Group "A"

1.

What will be the value of $x + xy$ according to Boolean **rule**?

Brief Answer Questions:

[10 × 1 = 10]

2.

Define Digital System.

Prove any statement of Demorgan theorem for **two** variable using truth table.

3.

4.

What is asynchronous counter?

5.

6.

Differentiate between positive edge **triggering** and **negative edge** triggering. **How the** number **of cell** is **determine** in a K-map?

7. Define ROM.

8.

Convert gray code: **1011 to** binary.

9.

Define POS.

10. **Define** shift register.

Group "B"

Short Answer Questions: (Attempt any *FIVE Questions*)

11. Convert (2A31)₁₆ into **decimal**, binary **and** octal form.
12. Realize **the** property of NOT, **NOR** and **AND** gate using **NAND** gate.
13. Compute $(-20)_{10} + (+30)_{10}$, **using** 2's complement method.
14. List out **the** design procedure of **combinational** circuit.
15. **Design** 1 x 4 D- multiplexer.
16. **Write the** expression in **SOP** for **the following** Karnaugh Map: .

AB/CD 00

11

10

00

1 1 0

1

01

10

0

x

11

10

x

*

*

11

0 0

x

[5×3 = 15]

Group "C"

Long Answer *Questions*: (Attempt any **THREE** Questions)

17. Design MOD-120 Asynchronous counter.

18. Design a circuit diagram for 3-bit binary adder.

19. What is bidirectional register? Explain with example.

44

[3×5=15]

20. Minimize the boolean function: $f(M, N, P, R) = (0, 3, 5, 7, 9, 10, 12, 15)$ with don't care condition $d(M, N, P, R) = \Sigma (2, 4, 6, 8)$ using K-map and design a circuit diagram with a simplified expression.

Group "D"

Comprehensive Answer / Case/Situation Analysis Questions:
[2x10=20]

21. Analyze the property of flip-flop which will have **indeterminate state** when set and reset inputs are "1" and illustrate the operational characteristics of flip-flop that solve the mentioned problem.

22. Design 8×3 Encoder. Analyze the number of don't care condition in the design of 8×3 encoder.