

Unit-4 Assignment-5 (Deadline August 5)

1. Do the Comparison between PROM, PAL, PLA.
2. Implement the following Boolean functions using PROM

$$F_1(A_1, A_0) = \Sigma m(1, 2) \quad F_2(A_1, A_0) = \Sigma m(0, 1, 3)$$

3. Implement the following function using PLA

$$A(x, y, z) = \Sigma m(1, 2, 4, 6)$$

$$B(x, y, z) = \Sigma m(0, 1, 6, 7)$$

$$C(x, y, z) = \Sigma m(2, 6)$$

4. Design a BCD to Excess 3 code converter and implement using suitable PLA.
5. Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number