



# Register


- Register is a type of memory element that store the data.
- Register has the combination of flip-flops.
- In order to increase the storing capacity of the register, the number of flip-flops used must be increased.
- The  $n$ -bit register consists of  $n$  number of flip-flops and is capable of storing  $n$ -bit words.
- The D flip-flop is used to make register as it gives same output as input.

# Shift Register


- Shift registers are a type of sequential logic circuit, mainly for storage of digital data.
- They are a group of flip-flops connected in a chain so that the output from one flip-flop becomes the input of the next flip-flop.
- All flip-flop is driven by a common clock, and all are set or reset simultaneously.
- There are two ways to shift data in to register and out of it, either serial or parallel.
- The SERIAL SHIFTING method shift one bit at a time for each clock.
- In PARALLEL SHIFTING all data gets shifted simultaneously.



## Types of Shift register

- Depending on the method of entering data and data retrieving process, it can be divided in four classes. They are as follows:
  - **SISO (Serial In Serial Out)**
  - **SIPO (Serial In Parallel Out)**
  - **PIPO (Parallel In Parallel Out) / Buffer**
  - **PISO (Parallel In Serial Out)**
- 
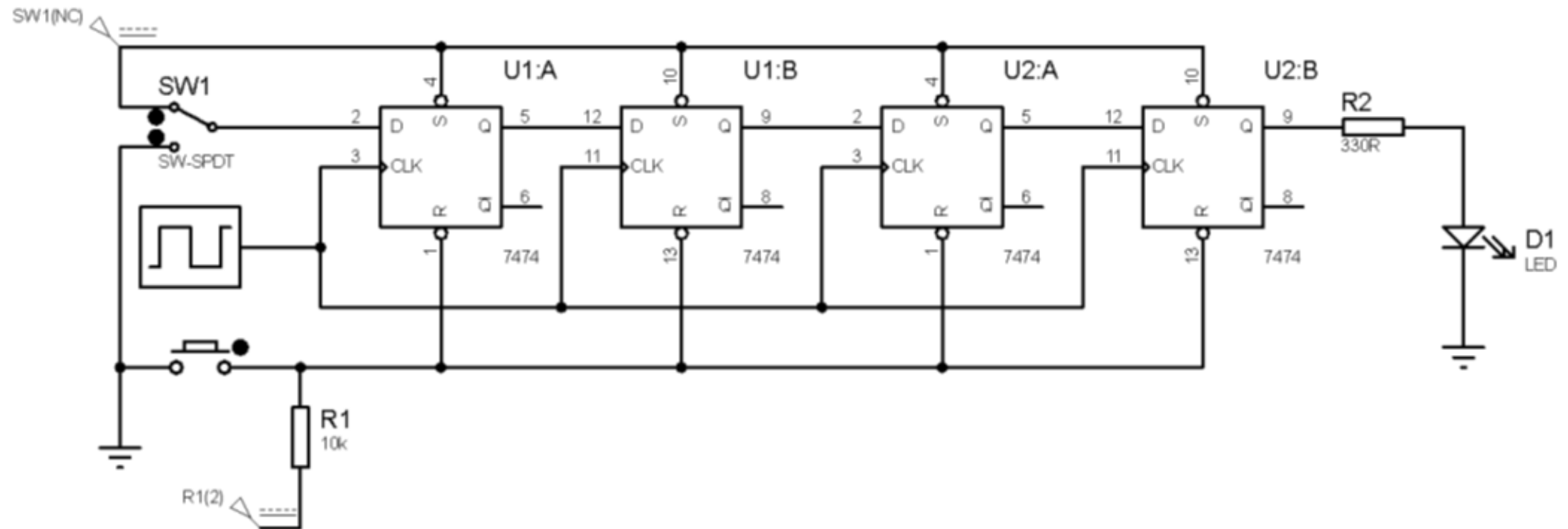
# Construction of 4-bit SISO register (Right shift)



# Functional Table

- Let the desired data to be operated be 1101, then the functional table and timing diagram of the circuit will be:

**Functional Table**


Clk	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	0	1	0
4	1	1	0	1
5	0	1	1	0
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

→ Data entered serially


1
0
1
1

→ Data out serially

## SISO Right Shift timing Diagram

 


# SISO Description

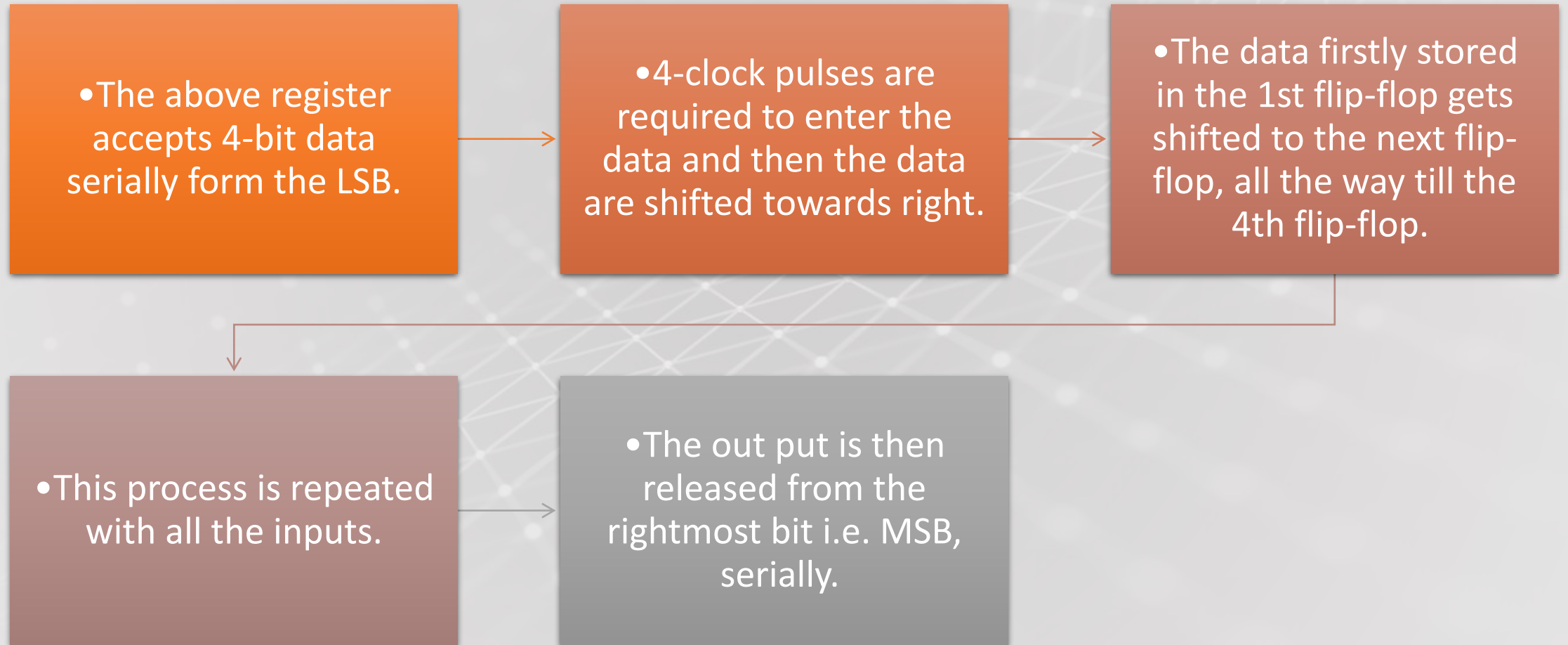


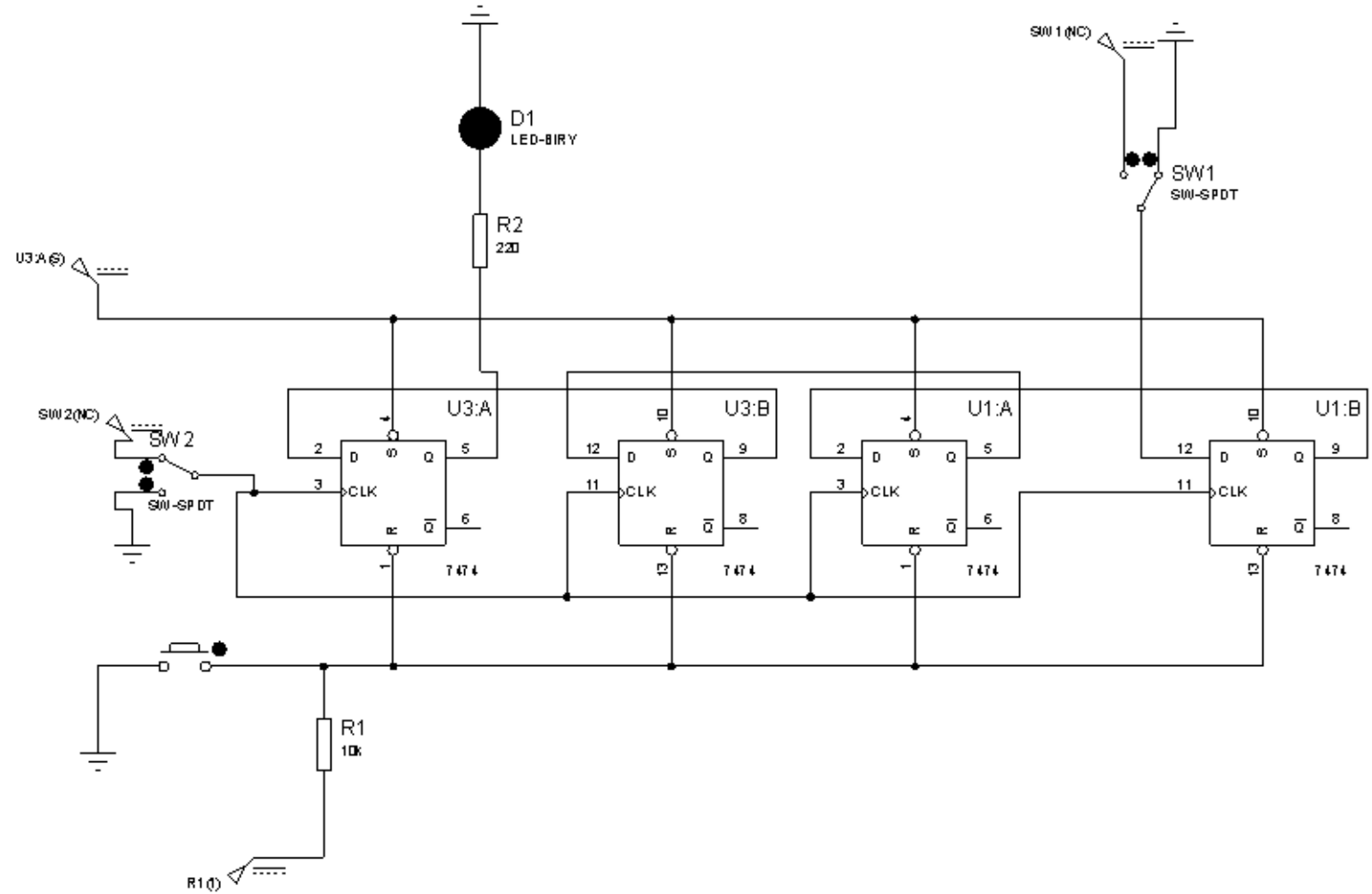
# Construction of 4-bit SISO register (Left shift)



## Functional Table (Left Shift)


**Functional Table**

Clk	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	1	0	1
4	1	0	1	1
5	0	1	1	0
6	1	1	0	0
7	1	0	0	0
8	0	0	0	0

1  
0  
1  
1

→ Data  
entered  
serially


# Timing Diagram Left Shift

 

## SIPO (Serial In Parallel Out)

- In this kind of register, data bits are entered serially in the same manner as in the SISO registers.
- The difference is the way in which the data bits are taken out of the register.
- Once the data are stored, each bit appears on its respective output line .
- All bits are available simultaneously.

# SIPO Practical Logic Diagram

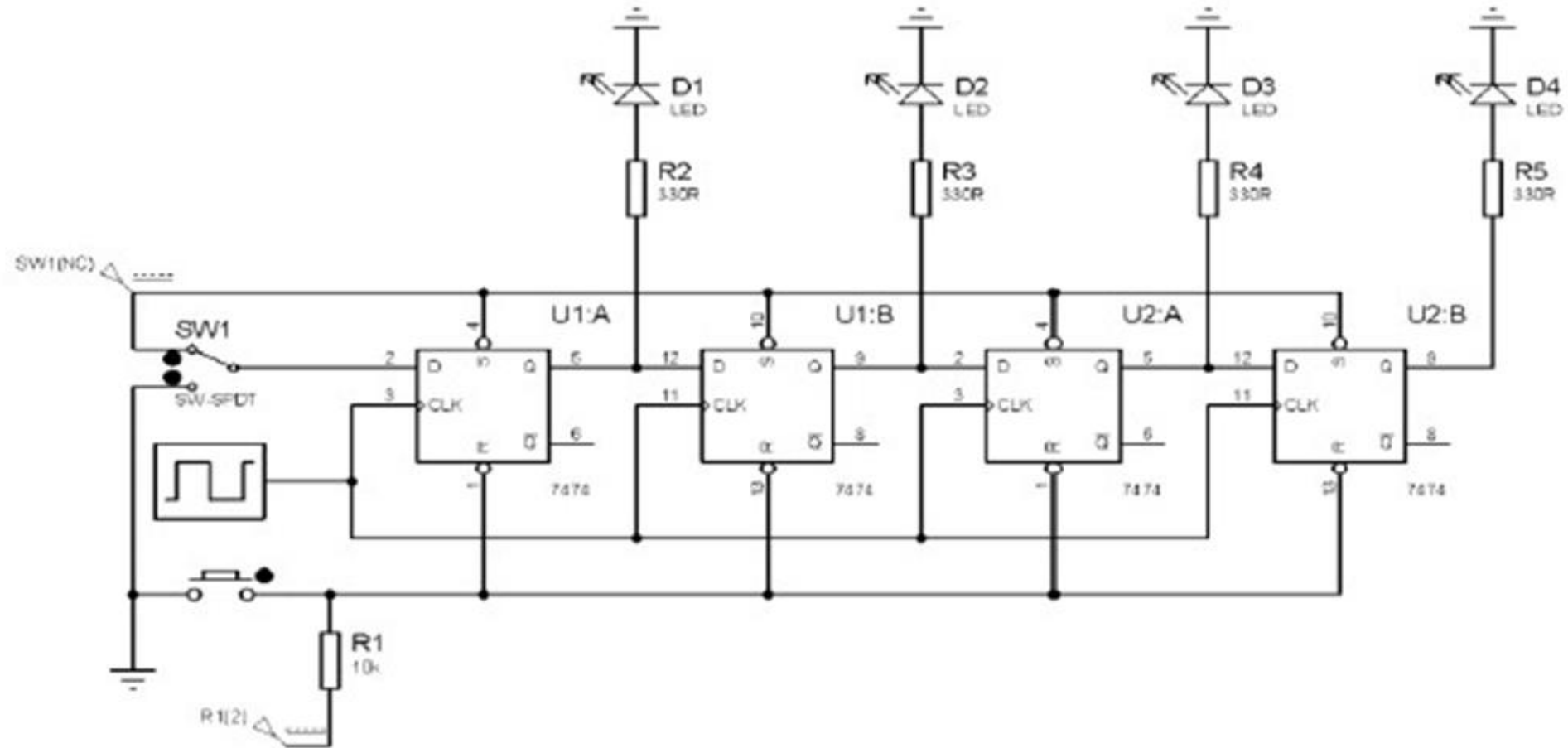

# SIPO

## Description

- In SIPO register 4-bit data are entered simultaneously like in the SISO.

- The data are shifted towards the left until the final bit of the data is entered.

- Once the entering and storing process is over, the data can be retrieved all at once .

- Then the data appears on the own output lines parallel.

# Functional Table

- Let the desired data to be operated be 1101, then the functional table and timing diagram of the circuit will be:

**Functional Table**


Clk	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	0	1	0
4	1	1	0	1

1 1 0 1

Data taken out parallelly

→ Data entered serially

# Timing Diagram

 




## PIPO (Parallel In Parallel Out) / Buffer

- In this register, the input is given in parallel and the output also collected in parallel.
- The clear (CLR) signal and clock signals are connected to all the 4 flip flops.
- Data is given as input separately for each flip flop and in the same way, output also collected individually from each flip flop.
- This type of shift register also acts as a temporary storage device or as a time delay device

# PIPO Practical Logic Diagram

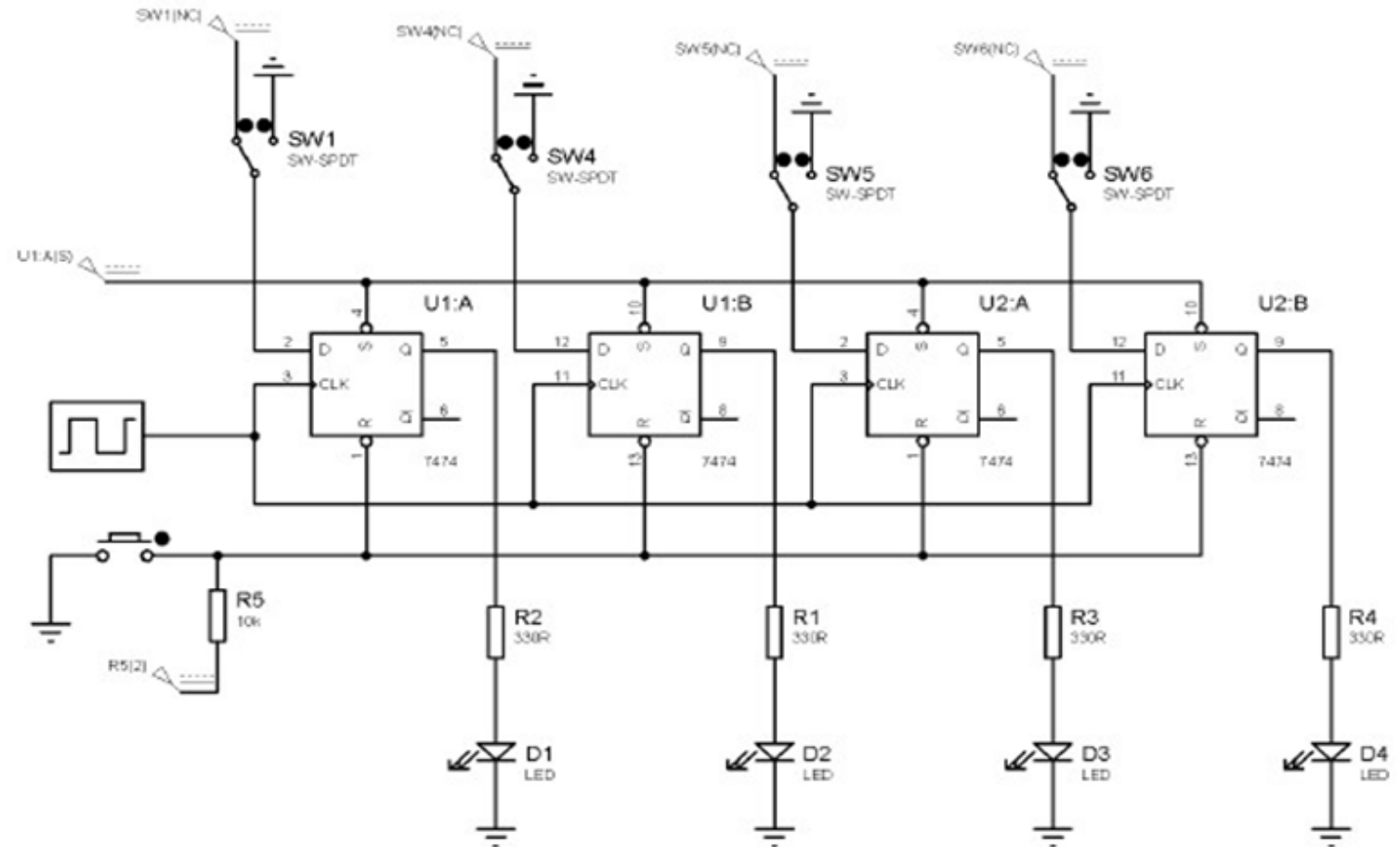

# PIPO

## Description

- In the above register, the inputs are given parallelly all at once and the outputs are also retrieved all at once.

- Once the register is clocked, all the data at the inputs appear at the corresponding outputs simultaneously.

- Let the desired data to be operated be 1101, then the functional table and timing diagram of the circuit will be:

- PIPO Functional Table

### Functional Table


Clk	$Q_0$	$Q_1$	$Q_2$	$Q_3$
<b>0</b>	0	0	0	0
<b>1</b>	1	1	0	1
	1	1	0	1

→ Data in parallelly

Data out parallelly

# Timing Diagram

## Timing Diagram

 

# PISO (Parallel In Serial Out)

- In parallel in - serial out shift registers, all data bits are loaded on the flip-flops immediately .

- However, the outputs are retrieved bit by bit.


- The data once stored in the flip-flops starts to shift in the adjacent flip-flop and the data are retrieved from the LSB.

- In order to make the circuit load the data and shift them, mode control input (shift/load') is used .

- which directs the circuit whether to parallelly load the data or serially shift them with the help of combination circuit.

- This combinational circuit consist of a pair of AND gates connected to the OR gate .

# PISO Practical logic Diagram

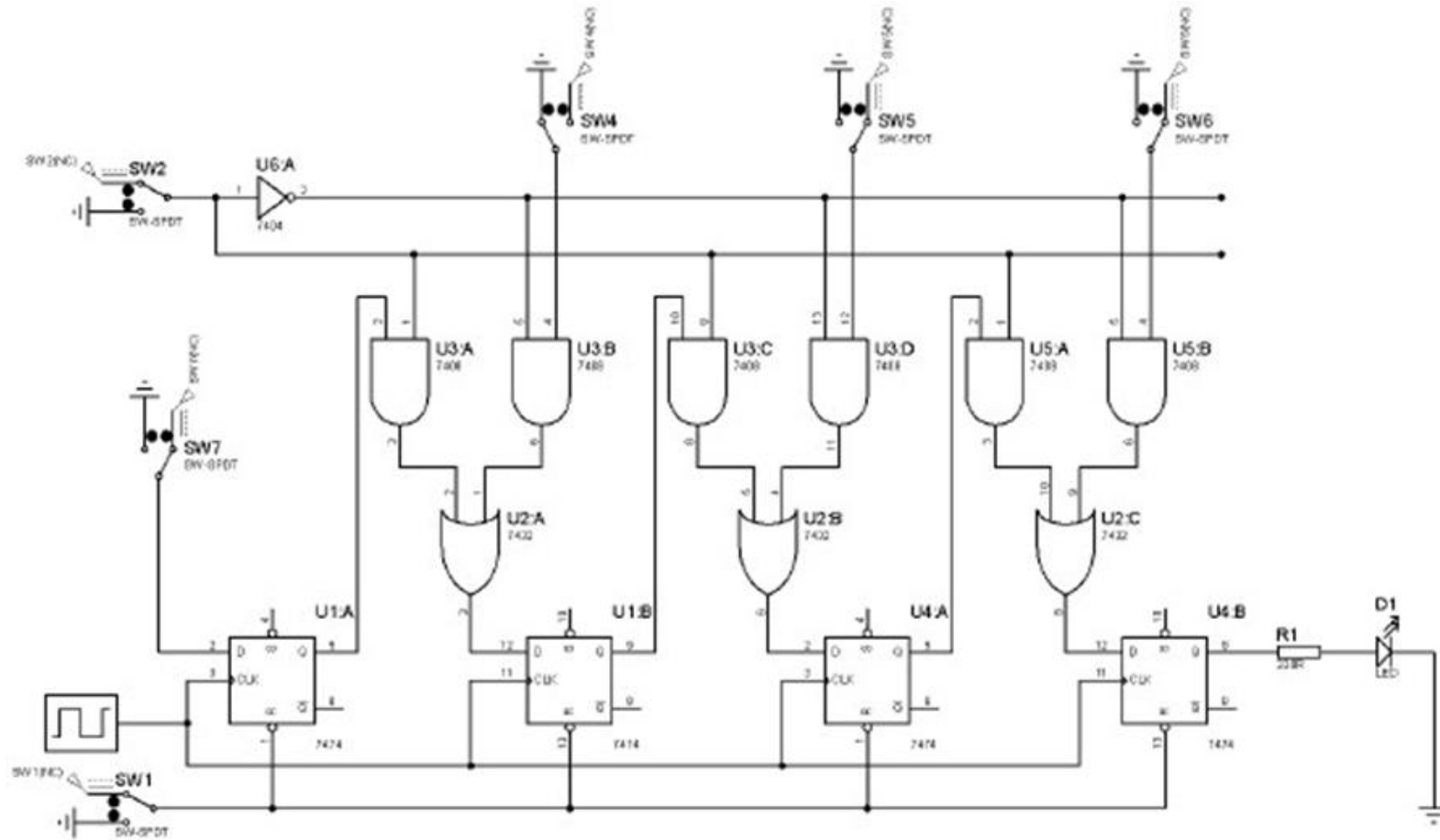

# PISO

## Description

- In the above circuit, firstly the control input is made low.
- Then the AND gate connected with the input signals get active passing the user's input to the flip-flop.
- Once the input process is over, the control input is made high.
- Then the AND gate connected with the output of previous flip-flop gets active allowing the outputs of the flip-flops to pass to the next flip i.e. shift towards next flip-flop.
- Through this shifting process, the data is retrieved bit by bit in a single line.



# Functional Table

- Let the desired data to be operated be 1101, then the functional table and timing diagram of the circuit will be:

**Functional Table**


C1k	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	1	0	1
2	0	1	1	0
3	0	0	1	1
4	0	0	0	1
5	0	0	0	0

← Data entered parallelly

1  
0  
1  
1

← Data taken out serially

# PISO Timing Diagram

 

# Shift Register Counter

- Two of the most common types of shift register counters are the Ring counter and the Johnson counter.

- They are basically shift registers with the serial outputs connected back to the serial inputs .

- In order to produce particular sequences.

- These registers are classified as counters because they exhibit a specified sequence of states.

# Ring Counter


- This circuit is basically a circulating shift register.
- The data moves in a ring.
- The output of the most significant stage i.e. last flip-flop is fed back to the input of the least significant stage i.e. first flip-flop.
- Initially before clock pulse, all the flip-flops except the first one are reset to 0 using clear and the first flip-flop is preset to 1 instead.
- An  $n$ -stage Ring counter yields a count sequence of length  $n$ , so it may be considered to be a mod- $n$  counter.



# Ring Counter Description

- The below 4-bit ring counter is constructed from four D flip-flops.
- The clock is provided in synchronous way in negative edge.
- The output of each stage is shifted into the next stage on the negative edge of a clock pulse serially.
- Initially, the ORI button is pushed which triggers the preset of 1st flip-flop and clear of rest flip-flops .
- The main advantage of this type of counter is that it is self-decoding.
- No extra decoding circuit is needed to determine what state the counter is in.

# Ring Counter Practical Diagram

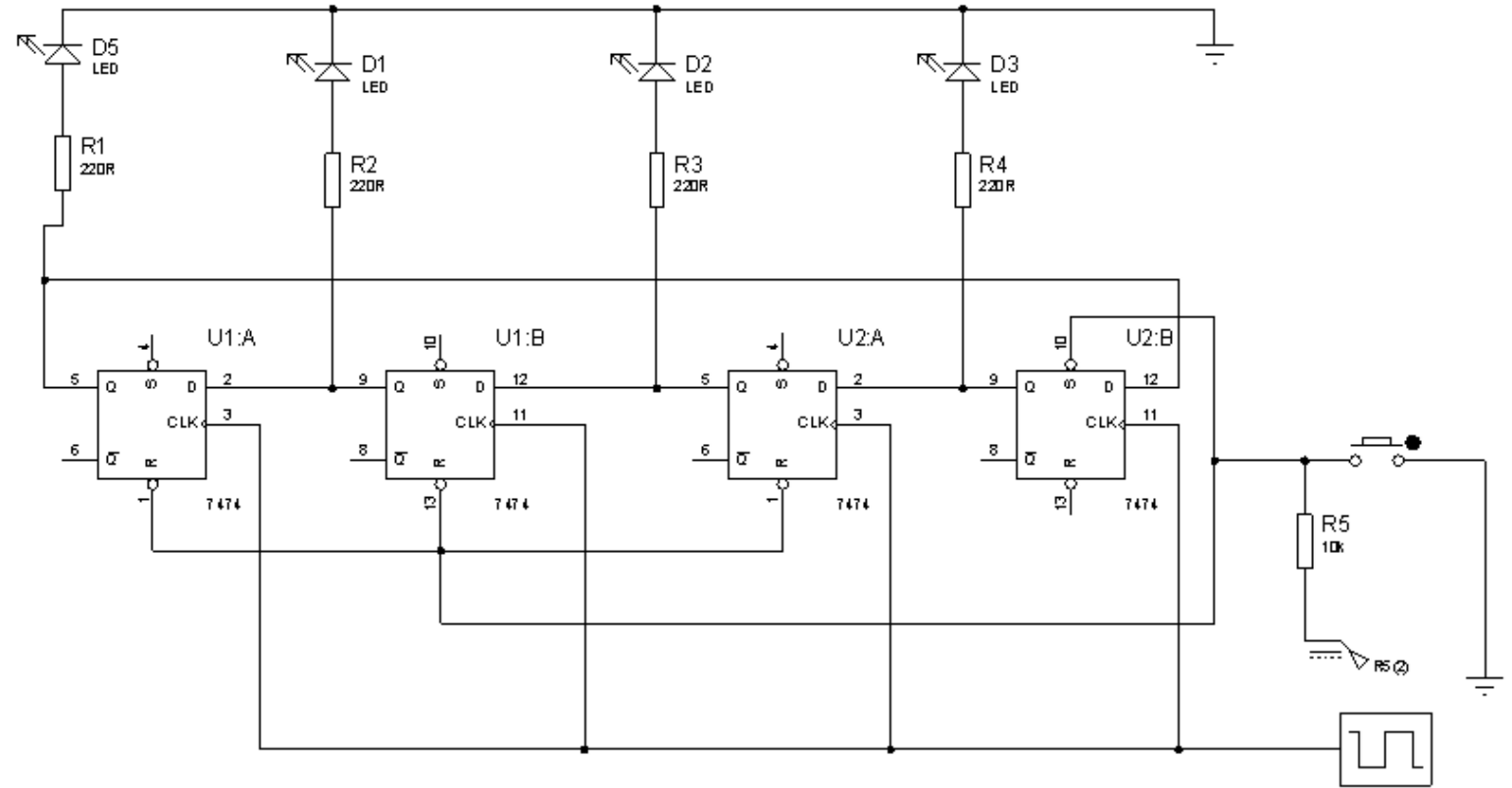


# Functional Table

- The functional table and timing diagram for the above 4-bit ring counter is as follows:

<b>ORI</b>	<b>Clk</b>	<b>Q<sub>0</sub></b>	<b>Q<sub>1</sub></b>	<b>Q<sub>2</sub></b>	<b>Q<sub>3</sub></b>
0	X	1	0	0	0
1	1	0	1	0	0
1	2	0	0	1	0
1	3	0	0	0	1
1	4	1	0	0	0

# Timing Diagram

Ring Counter

 




# Johnson Counter

- This circuit is also a circulating shift register.
- The data moves in a ring.
- These are a variation of standard ring counters, with the inverted output of the last stage fed back to the input of the first stage.
- They are also known as twisted ring counters.
- An  $n$ -stage Johnson counter yields a count sequence of length  $2n$ , so it may be considered to be a mod- $2n$  counter.
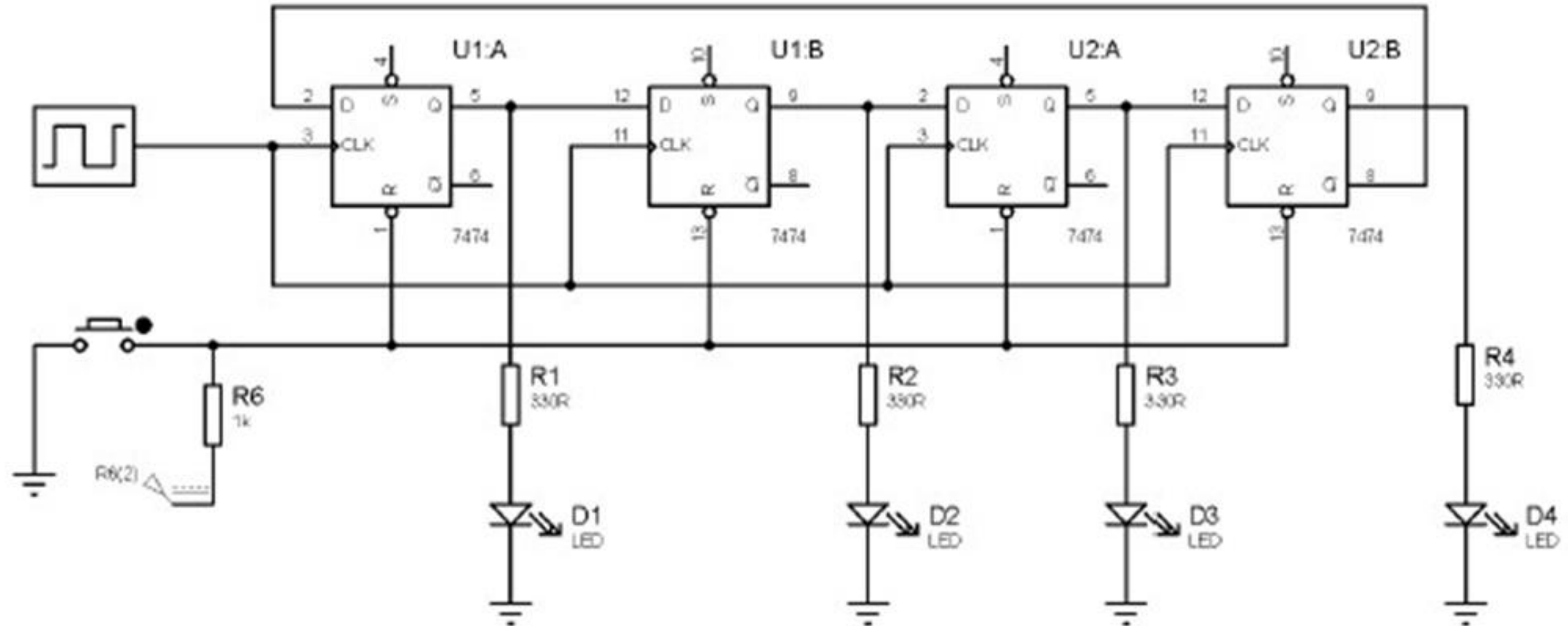
# Johnson Counter Practical Logic Diagram



# Johnson Counter description

- the above 4-bit Johnson counter is constructed from four D flip-flops.
- The clock is provided in synchronous way in negative edge.
- The output of each stage is shifted into the next stage on the negative edge of a clock pulse serially.
- Initially, the Clr button is pushed which triggers the clear of all flip-flops.
- This type of counter is also a self-decoding circuit.
- No extra decoding circuit is needed to determine what state the counter is in.


# Functional Table

The functional table and timing diagram for the above 4-bit Johnson counter is as follows:

**Functional Table**

<b>Clr</b>	<b>Clk</b>	<b>Q<sub>0</sub></b>	<b>Q<sub>1</sub></b>	<b>Q<sub>2</sub></b>	<b>Q<sub>3</sub></b>
<b>0</b>	X	0	0	0	0
<b>1</b>	1	1	0	0	0
<b>1</b>	2	1	1	0	0
<b>1</b>	3	1	1	1	0
<b>1</b>	4	1	1	1	1
<b>1</b>	5	0	1	1	1
<b>1</b>	6	0	0	1	1
<b>1</b>	7	0	0	0	1

# Timing Diagram

 

# Applications of Shift Registers

Registers are used in digital electronic devices like computers as:

- <sup>®</sup> Temporary data storage
- <sup>®</sup> Data transfer
- <sup>®</sup> Data manipulation
- <sup>®</sup> As counters

# Applications of Shift Registers (Contd)

- 1.Shift registers are used in computers as memory elements. All the digital systems need to store large amount of data, in an efficient manner; there we use storage elements like RAM and other type of registers.
- 2.Many of the digital system operations like division, multiplication, are performed by using registers. The data is transferred through serial shift registers and other type.
- Serial in – serial out registers are used for time delays.
- <sup>®</sup> Serial in – parallel out registers are used for converting the data from serial form to parallel form.
- <sup>®</sup> Parallel in – serial out registers are used for converting the data from parallel form to serial form.